

# Chapter 9


# Memories

---

關志達

台灣大學電機系

# Categories of Memory Arrays

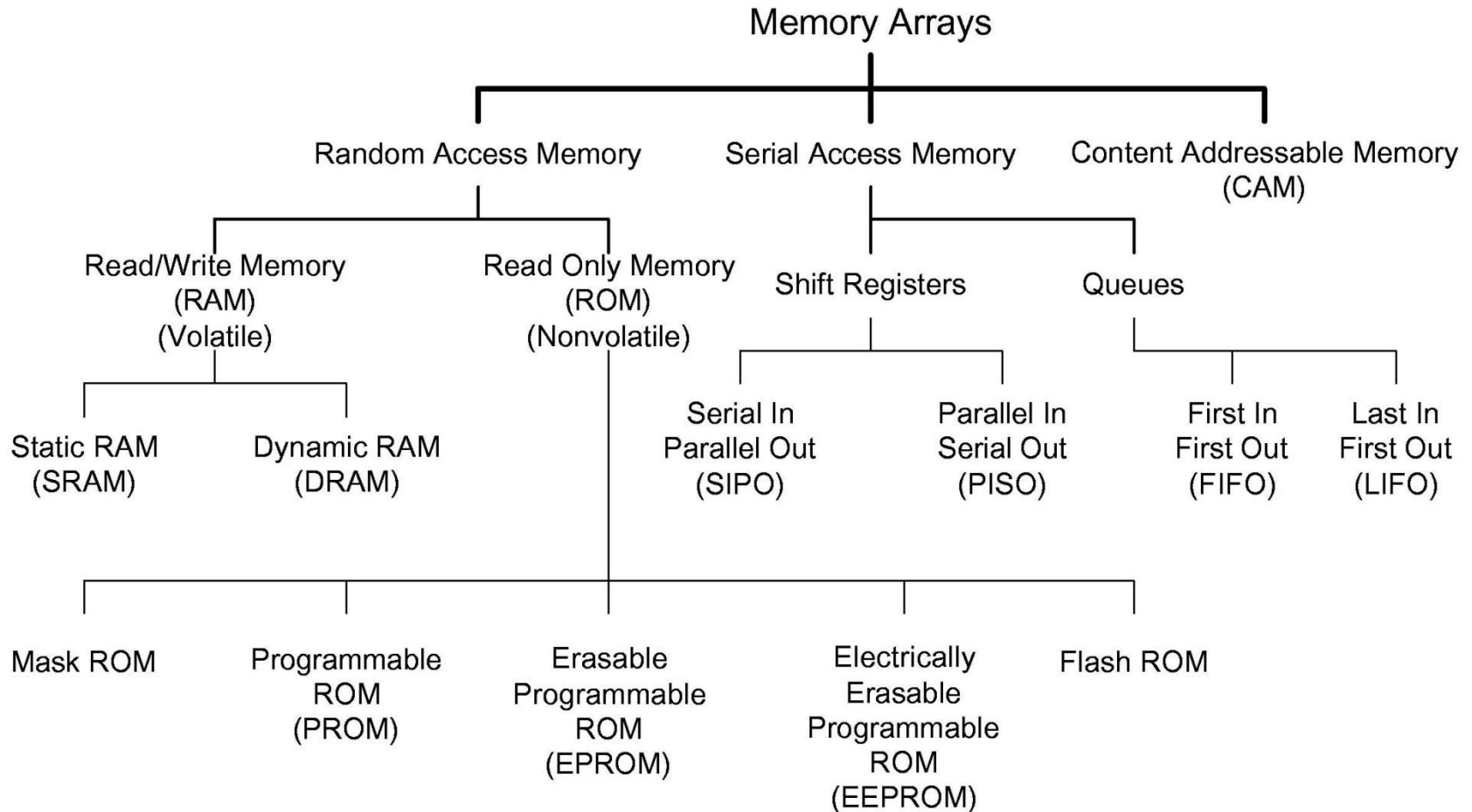




# Introduction

---

- Category of random access memory
  - ROM (read-only memory)
    - Nonvolatile
    - Mask ROM, EPROM, EEPROM, Flash (variant of EEPROM, erases entire blocks rather than individual bits)
  - RAM (read/write memory)
    - Volatile
    - Static vs. dynamic structures
    - Area, speed, leakage, cost tradeoff
- Memory cells can have one or more ports for access
 
# Array Architecture



- $2^n$  words of  $2^m$  bits each
- If  $n \gg m$ , fold by  $2^k$  into fewer rows of more columns



- Good regularity - easy to design
- Very high density if good cells are used

  
# 12T SRAM Cell

- Basic building block: SRAM Cell
  - Holds one bit of information, like a latch
  - Must be read and written
- 12-transistor (12T) SRAM cell
  - Use a simple latch connected to bitline




 
# 6T SRAM Cell

- Cell size accounts for most of array size
  - Reduce cell size at expense of complexity
- 6T SRAM Cell
  - Used in most commercial chips
  - Data stored in cross-coupled inverters
- Read
  - Precharge bit, bit\_b
  - Raise wordline
- Write
  - Drive data onto bit, bit\_b
  - Raise wordline



 
 
# SRAM Read

- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex:  $Q=0$ ,  $Q_b=1$ 
  - bit discharges, bit\_b stays high
  - But Q bumps up slightly
- Read stability
  - Q must not flip
  - $N1 \gg N2$


  
# SRAM Write


- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex:  $Q=0$ ,  $Q_b=1$ ,  $\text{bit}=1$ ,  $\text{bit}_b=0$ 
  - Force  $Q_b$  low, then  $Q$  rises high
- Writability
  - Must overpower feedback inverter
  - $N2 \gg P1$





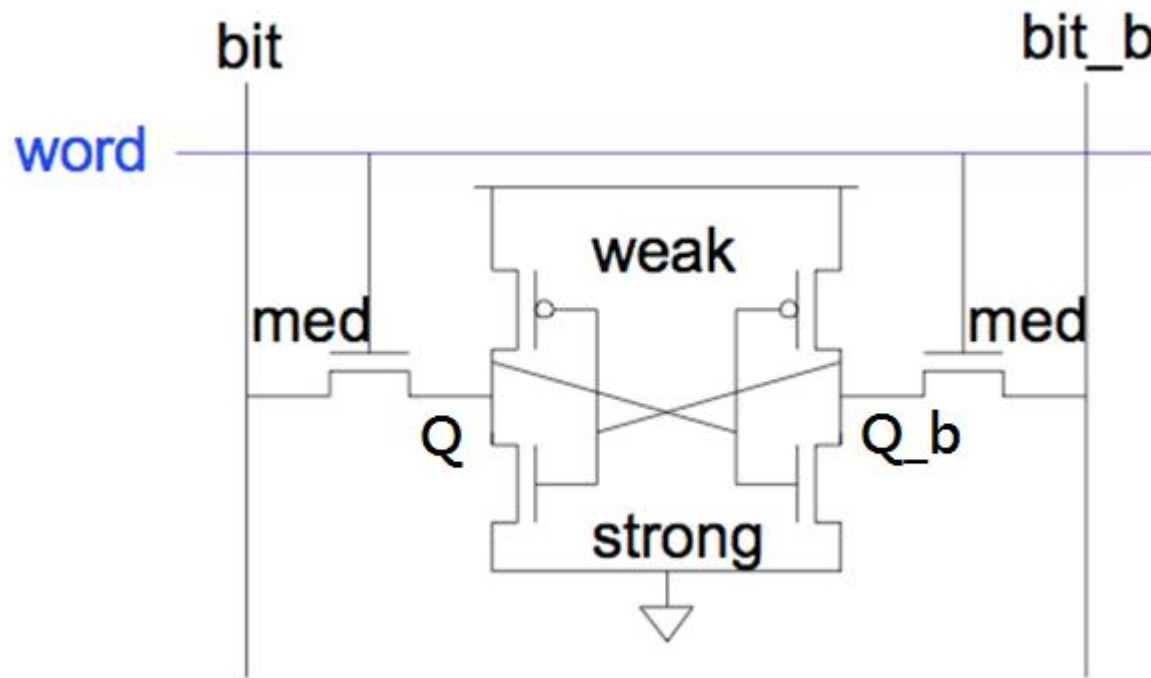
# SRAM Sizing

- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell





# SRAM Column Example


## Read

 

## Write

  


# Another SRAM Write Circuit


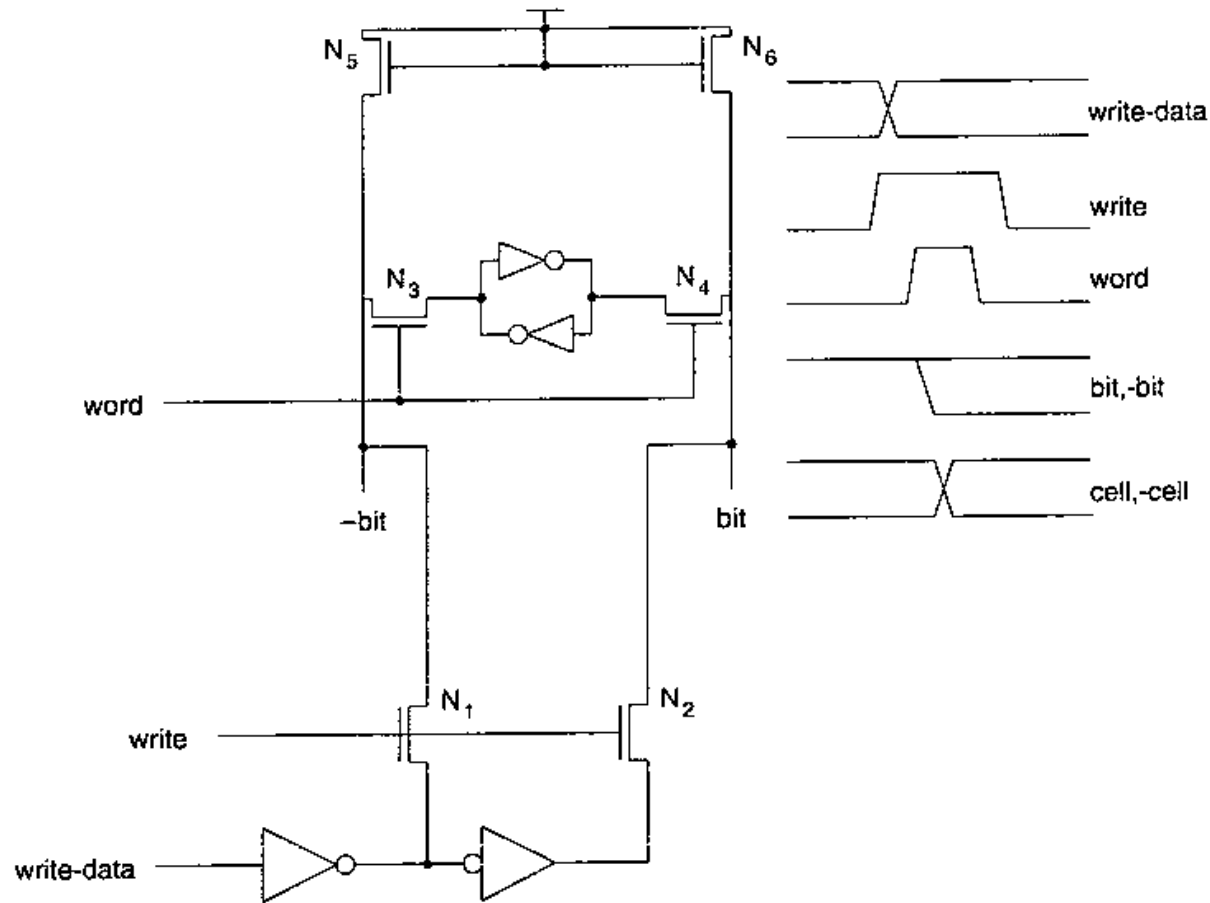

 
# Decoders


- $n:2^n$  decoder consists of  $2^n$   $n$ -input AND gates
  - One needed for each row of memory
  - Build AND from NAND or NOR gates



static CMOS

  


pseudo nMOS

 

 
# Large Decoders

- For  $n > 4$ , NAND gates become slow
  - Break large gates into multiple smaller gates


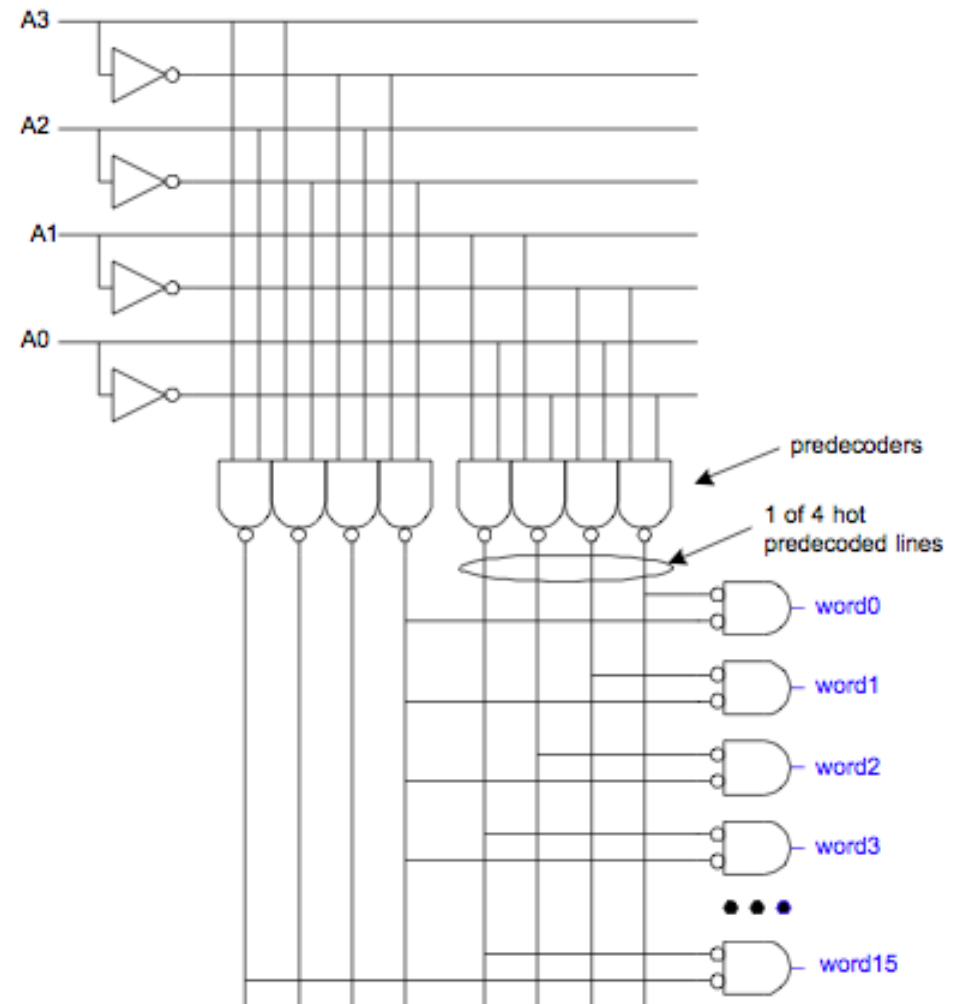
# Predecoding

- Many of these gates are redundant
  - Factor out common gates into predecoder
  - Saves area






# Column Circuitry

---


- Some circuitry is required for each column
  - Bitline conditioning
  - Sense amplifiers
  - Column multiplexing

# Bitline Conditioning

- Precharge bitlines high before reads

 

 - Equalize bitlines to minimize voltage difference and thus ensure correct sensing using sense amplifiers








# Sense Amplifiers

---


- Bitlines have many cells attached
  - Ex: 64-kbit SRAM has 256 rows x 256 cols
  - 256 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$ 
  - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce  $\Delta V$ )

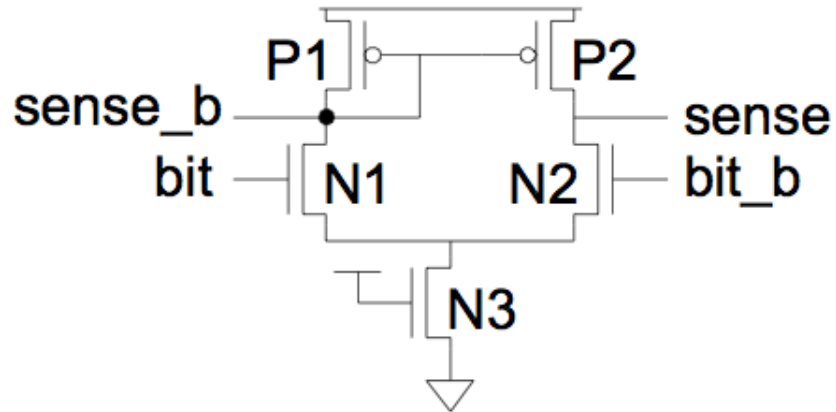- Differential pair requires no clock
- But always dissipates static power


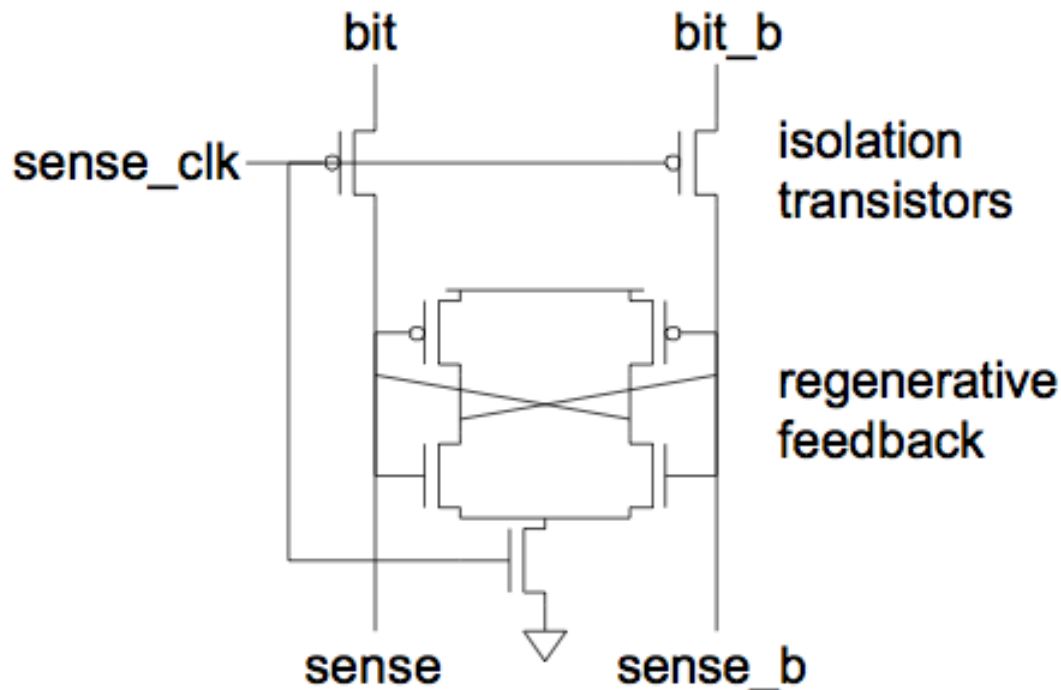
# Clocked Sense Amp

- Clocked sense amp saves power
- Requires sense\_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance during sensing






# Column Multiplexing

---

- Recall that array maybe folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - Must select 16 output bits from the 128 columns
  - Requires 16 8:1 column multiplexers

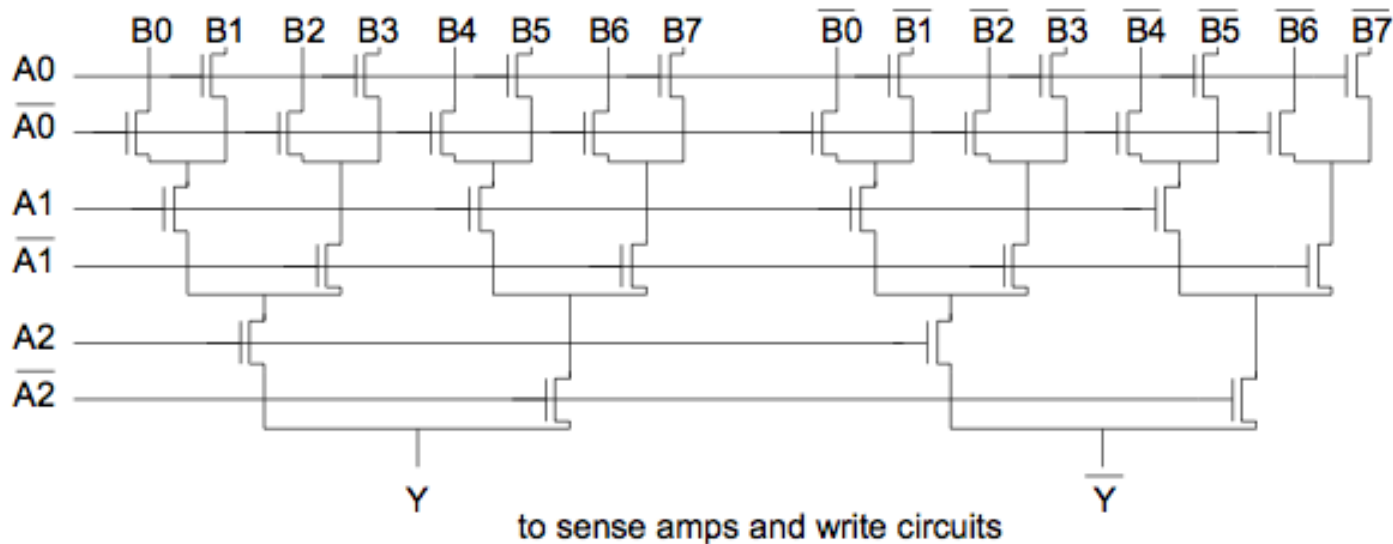
# Tree Decoder MUX

- Column mux can use pass transistors
  - Use NMOS only
- One design is to use k series transistors for  $2^k:1$  mux
  - No external decoder logic needed


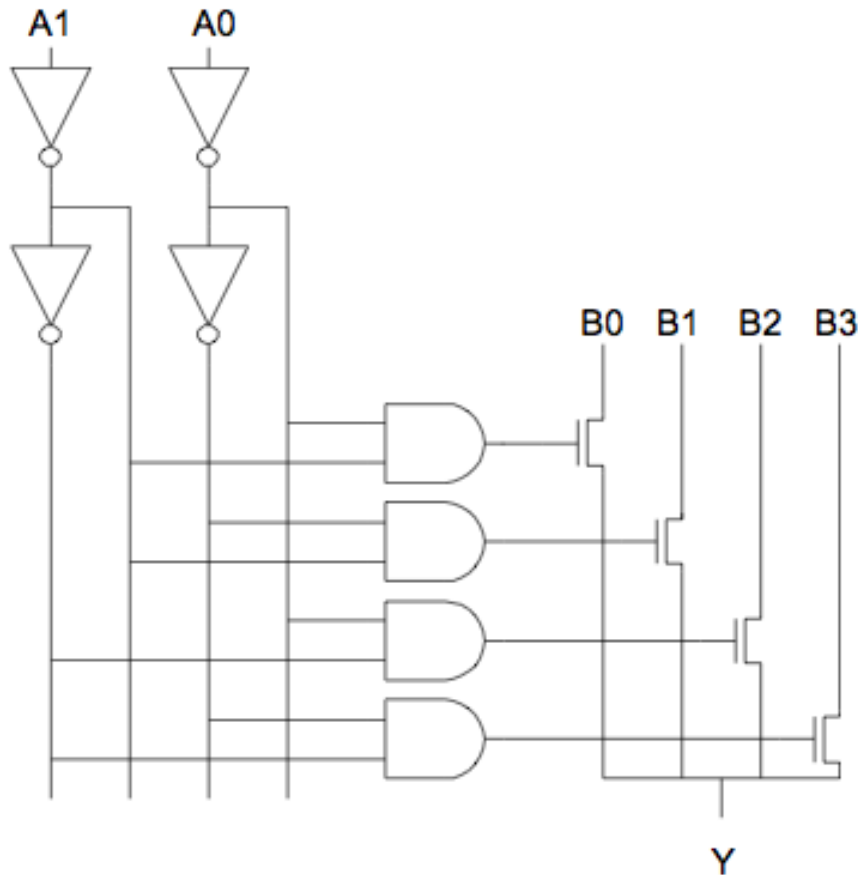
# Single Pass-Gate MUX

- Eliminate series transistors with separate decoder to do the binary-unary decoding.






# Multiple Ports

---

- We have considered single-ported SRAM
  - One read or one write on each cycle
- Multiported SRAM are needed for register files
- Examples:
  - Pipelined processor must read two sources and write a third result each cycle
  - Superscalar processor must read and write many sources and results each cycle
 
# Dual-Ported SRAM

- Simple dual-ported SRAM
  - Two independent single-ended reads
  - Or one differential write




- Do two reads and one write by time multiplexing
  - Read during  $\phi 1$ , write during  $\phi 2$



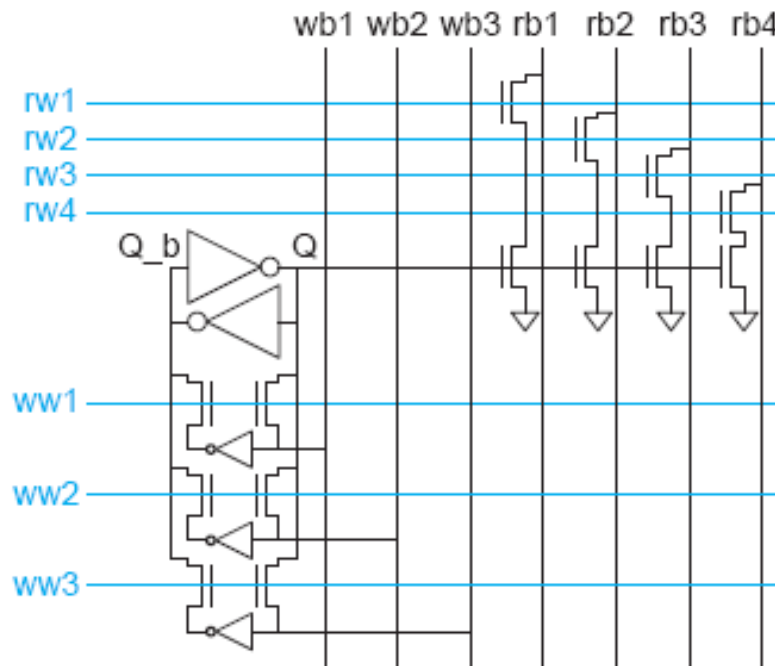
# Multi-Ported SRAM

- Add more access transistors hurts read stability
- Multiported SRAM isolates reads from state nodes
- Single-ended design minimizes number of bitlines




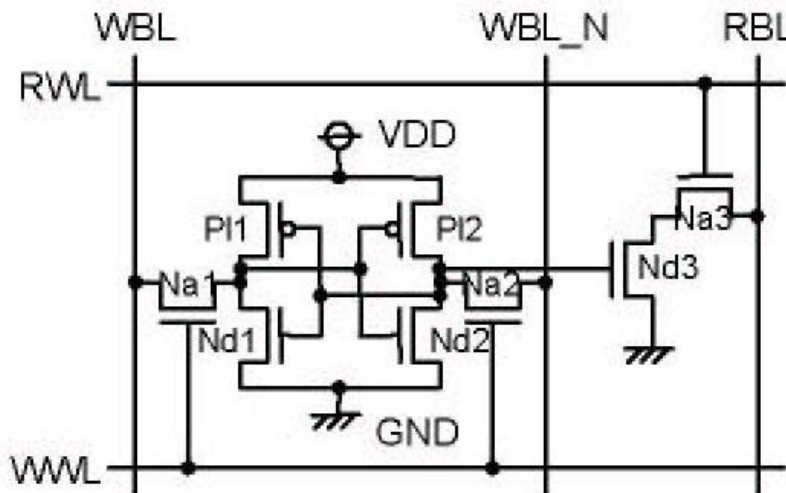
# Future Trend

- Use 8T SRAM cell in 65nm-32nm technology
  - Morita VLSI Circuits Symp. 2007.
  - Separate read port from write port
  - Can support Vdd down to 0.42V



 
 
# Dynamic RAM

- Cell charge is dynamic and cell needs periodically refreshing
- Destructive reading and voltage swing is very small.
- Bit lines are precharge to  $V_{DD}/2$ .
- $\Delta V = (V_{DD}/2)[C_{cell}/(C_{cell} + C_{bit})]$


  
# DRAM

- Trench capacitor can drastically decrease the cell area
- Schematic and scanning electron microscope (SEM) photo.





# Read-Only Memories


---

- Read-only memories are nonvolatile
  - Retain their contents when power is removed
- Mask-programmed ROMs use one transistor per bit
  - Presence or absence determines 1 or 0

# ROM Example

- 4-word x 6-bit ROM

- Represented with dot diagram
- Dots indicate 1's in ROM

 


Word 0: **010101**

Word 1: **011001**

Word 2: **100101**




Word 3: **101010**

 

Looks like 6 4-input pseudo-nMOS NORs
   
# NAND ROMs

- Smaller area due to no ground lines.
- Cell area can be further reduced by eliminating the contacts and using an extra implant step that makes the  $V_{th}$  negative and turns on the transistor permanently.




# PROMs and EPROMs

## ■ Programmable ROMs

- Build array with pull-down transistors at every site
- Burn out fuses to disable unwanted transistors; one-time programmable (OTP).
 
## ■ Erasable Programmable ROMs

- Use floating gate to turn off unwanted transistors
- Negative charges are drawn into the isolated floating gate, which effectively increases the threshold voltage and turns off the transistor.
- EPROM, EEPROM, Flash








# Serial Access Memories

---

- Serial access memories do not use an address
  - Shift registers
  - Serial In Parallel Out (SIPO)
  - Parallel In Serial Out (PISO)
  - Queues (FIFO, LIFO)

 
# Shift Register

- Shift register store and delay data
- Simple design: cascade of registers
  - Watch your hold times, i.e., the signal may travel too fast.



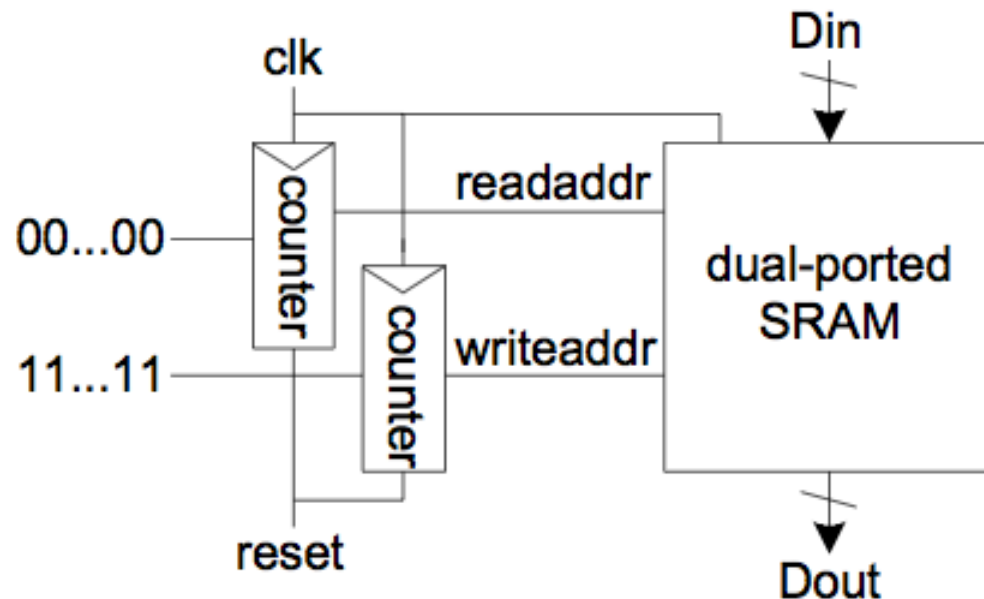
# Dense Shift Registers

- Flip-flops are not very area-efficient
- For large shift registers, keep data in SRAM instead
- Move read/write pointers to RAM rather than data
  - Initialize read address to first entry, write to last
  - Increment address on each cycle
  - Can use ring counters to replace counters and address decoders



 
# Serial In Parallel Out

- 1-bit shift register reads in serial data
  - After N steps, presents N-bit parallel output



 
# Parallel In Serial Out

- Load all N bits in parallel when shift=0
  - Then shift one bit out per cycle


 
# Queues

- Queues allow data to be read and written at different rates
- Read and write each use their own clock and data
- Queue indicates whether it is full or empty
- Build with SRAM and read/write counters (pointers)







# FIFO, LIFO Queues

---

- First In First Out (FIFO)
  - Initialize read and write pointers to first element
  - Queue is EMPTY
  - On write, increment write pointer
  - If write almost catches read, Queue is FULL
  - On read, increment read pointer
- Last In First Out (LIFO)
  - Also called a stack
  - Use a single stack pointer for read and write
  
# Content Addressable Memory


- Read and write memory as usual
- A content addressable memory takes in a data word and compare it with stored words and generates a match signal, which can be used to address a RAM. This is how the translation look-aside buffer works in a cache.




 
# 10-T CAM Cell

- Add four match transistors to 6T SRAM
- Match line will be pulled low when 'cell' and 'bit' mismatch.



# CAM Cell Operation


- Read and write like ordinary SRAM

- For matching:

- Leave wordline low
- Precharge matchlines
- Place key on bitlines
- Matchlines evaluate

- Miss line

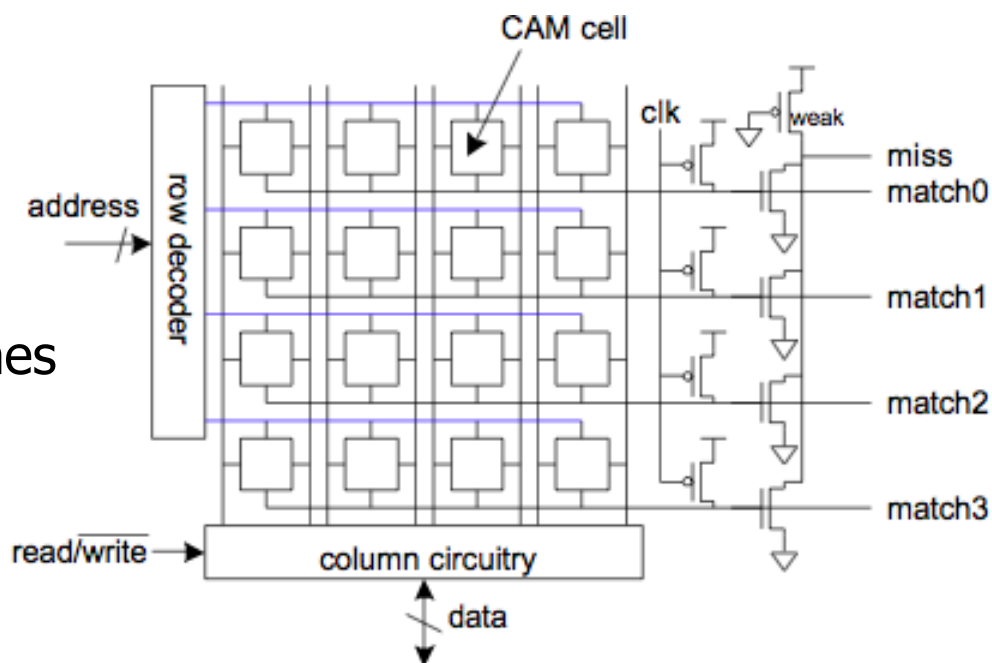- Pseudo-nMOS NOR match lines
- Goes high if no words match




# PLAs

- A Programmable Logic Array performs any function in sum-of-products form
- Literals: inputs & complements
- Products/Minterms: AND of literals
- Outputs: OR of Minterms
- Example: Full Adder



$$s = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$

$$c_{out} = ab + bc + ac$$

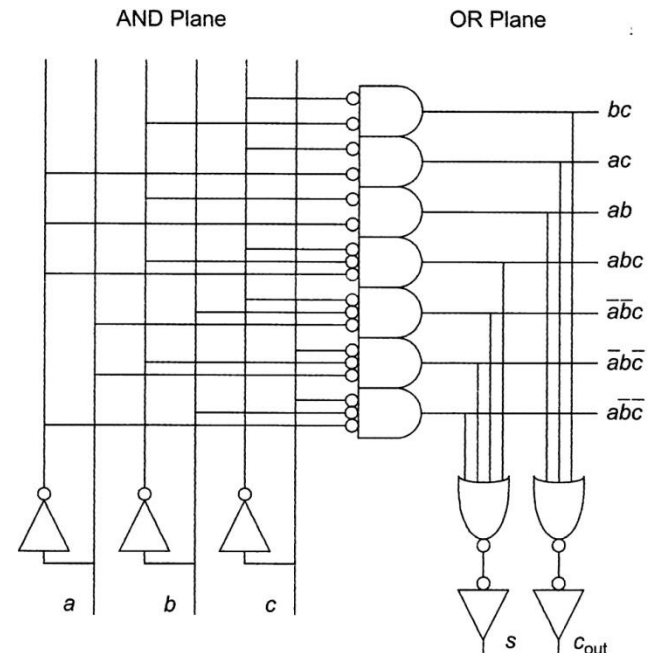

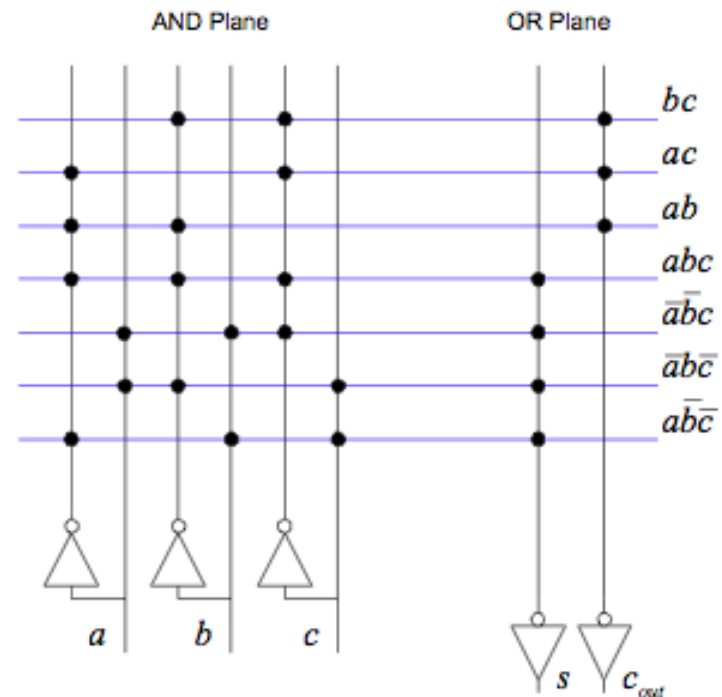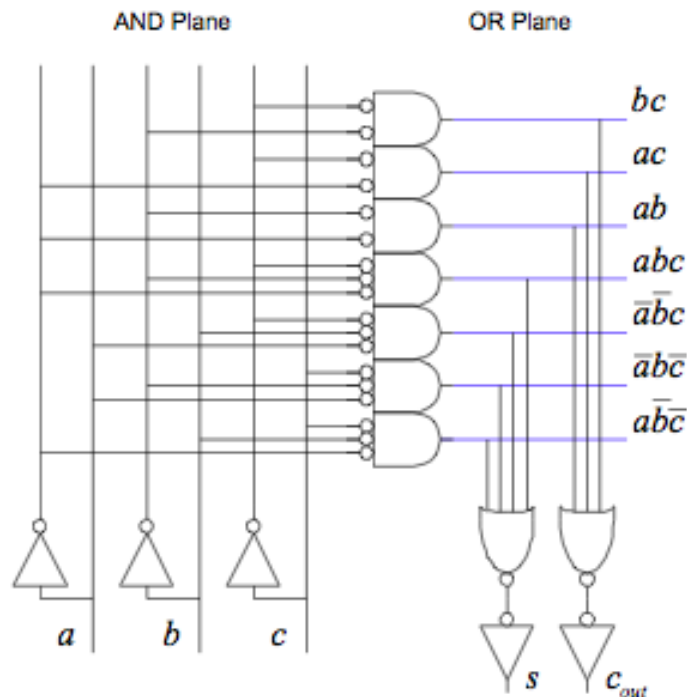
# NOR-NOR PLAs

- ANDs and ORs are not very efficient in CMOS
- Dynamic or Pseudo-nMOS NORs are very efficient
- Use DeMorgan's Law to convert to all NORs


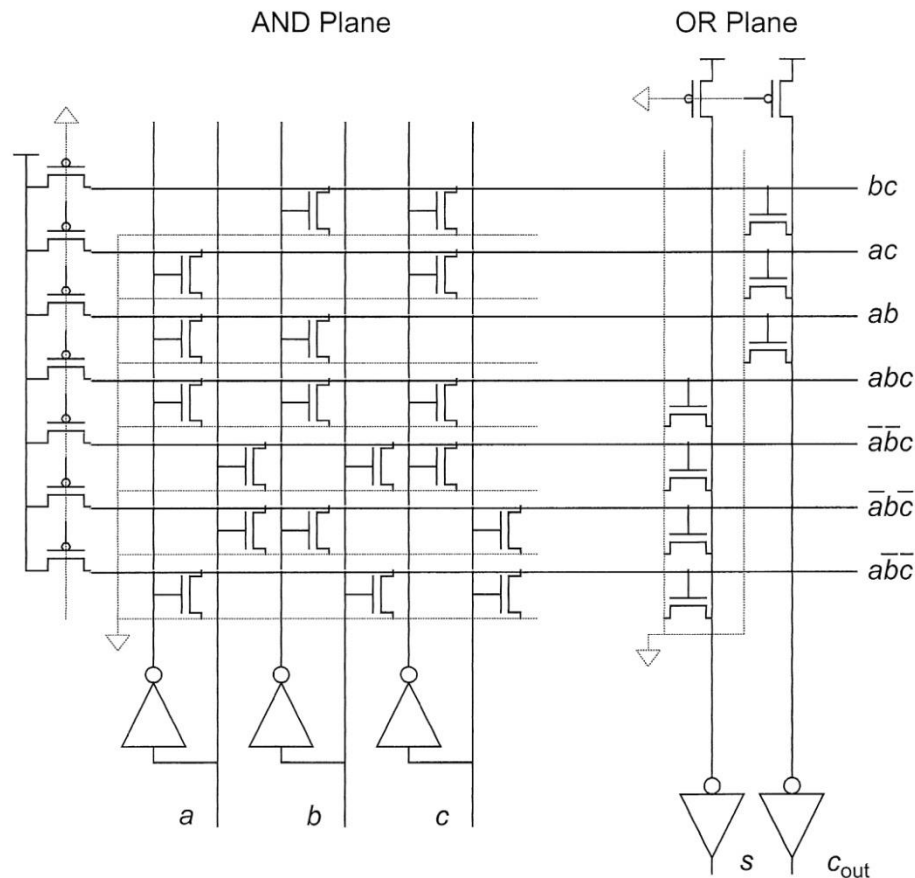
# PLA Schematic

- Pseudo-NMOS version
- Dynamic and self-timed version can be faster.





# PLAs vs. ROMs

---

- The OR plane of the PLA is like the ROM array
- The AND plane of the PLA is like the ROM decoder
- PLAs are more flexible than ROMs
  - No need to have  $2^n$  rows for  $n$  inputs
  - Only generate the minterms that are needed
  - Take advantage of logic simplification