

# Chapter 3

## Speed (Delay)


---

關志達

台灣大學電機系
 
# Delay in Circuits


- **Propagation delay** time,  $t_{pd}$  = **maximum** time between input transition (50%) to output crossing 50% output level.
  - $t_{pdf}$ ,  $t_{pdr}$
- **Contamination delay** time,  $t_{cd}$  = **minimum** time between input transition (50%) to output crossing 50% output level.
- When a signal travels with contamination delay and violate hold time of the following FF, the output value may be "contaminated" by the faster-than-normal signal. This condition is called "**race**."



# Transition Times

- **Rise time**,  $t_r$  = time for a waveform to rise from 20% to 80% of its steady-state value.
- **Fall time**,  $t_f$  = time for a waveform to fall from 80% to 20% of its steady-state value.
- Average transition time,

$$t_{rf} = (t_r + t_f)/2$$

 



# Gate RC Delay Estimation




---

- Delay of a gate is inversely proportional to its driving strength ( $1/R$ ) and proportional to its load capacitance ( $C$ ).
- Note that we can assume PMOS needs be **twice** as wide as NMOS to get same driving strength. Assume  $\mu_n = 2\mu_p$
- Resistor
  - ON transistor can be modeled as a resistor.
- Capacitance
  - Gate capacitance
  - Diffusion capacitance
  - Wire capacitance


# RC Analysis Example

**W: transistor width**

**All transistors have same L**

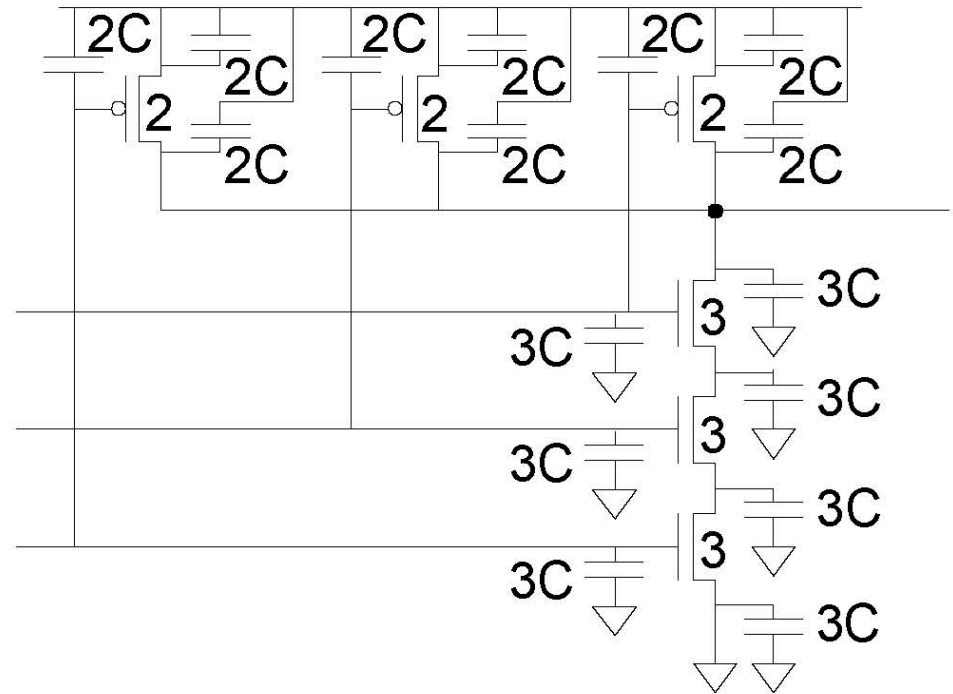  

# Equivalent Circuit with RC

 


**Treat Vdd as AC GND**

# Elmore Delay Model

- Pull-up and pull-down network are like RC ladder
- R is on the **shared path** from the **source** to the **node** and the **leaf** (the node to compute delay).


$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$




# Elmore Delay Model Examples

## ■ Compute $V_{out3}$

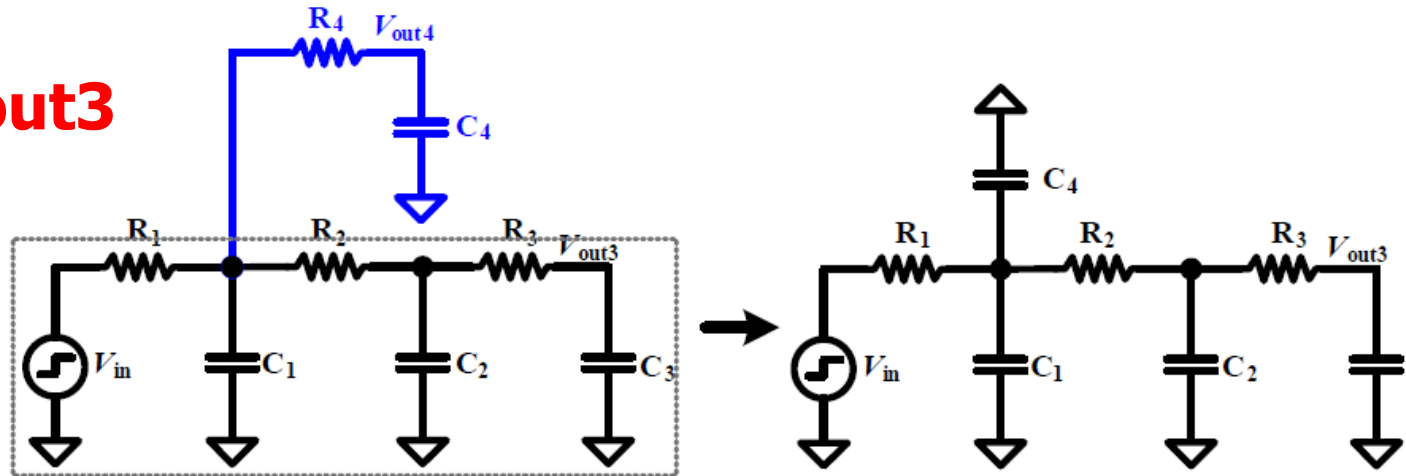

## ■ Compute $V_{out4}$

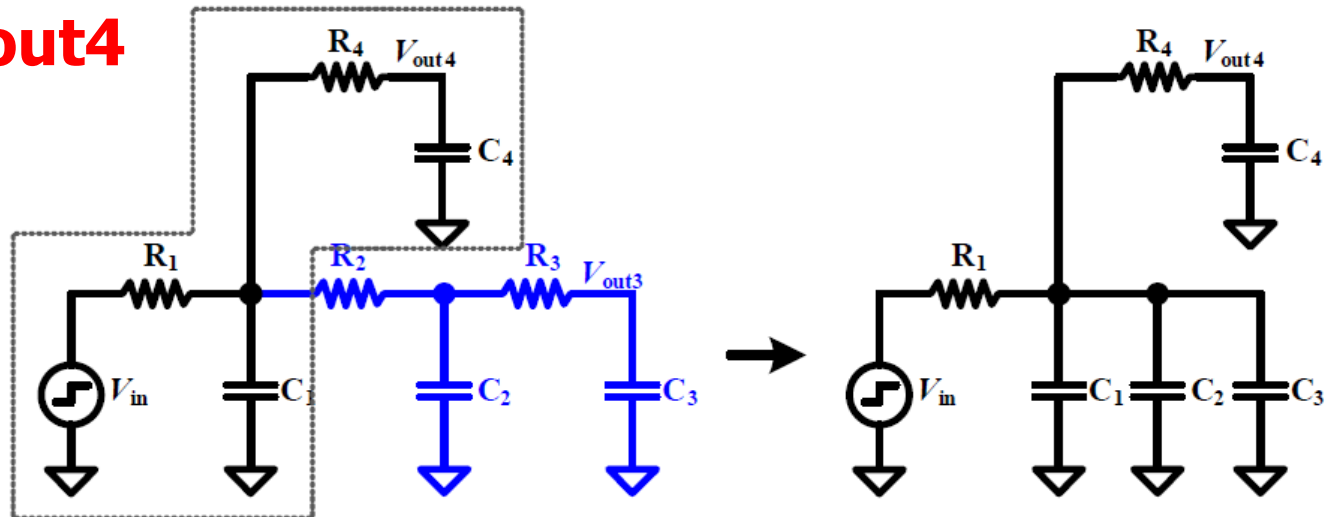




# Delay Analysis Example



- 3-input NAND, no load

When Y goes LOW

 

$$\begin{aligned} t_{pdf} &= R(9C) + (2R/3)(3C) + (R/3)(3C) \\ &= \underline{12RC} \end{aligned}$$


When Y goes HIGH

  

$$\begin{aligned} t_{pdr} &= R(9C) + R(3C) + R(3C) \\ &= \underline{15RC} \end{aligned}$$

 
# Loaded Analysis

- $h$  is the number of fanout 3-input NAND gates



$$t_{pdf} = R(9C + 5hC) + (2R/3)(3C) + (R/3)(3C)$$

$$= \underline{(12 + 5h)RC}$$

 

$$t_{pdr} = R(9C + 5hC) + R(3C) + R(3C)$$

$$= \underline{(15 + 5h)RC}$$


# Linear Delay Model

- A common delay estimation approach in IC design is to treat logic gates as simple delay elements with the following delay time

$$t_{pd} = t_{internal} + t_{LE} * h = p + g * h$$

where  $t_{internal}$  is the fixed parasitic internal delay and  $t_{LE}$  is the unit-output-loading logical effort delay;  $h$  is the number of fanout gates of the same type. For different type of gates,  $h = C_L/C_{in} = C_{out}/C_{in}$ .
 
$$\begin{aligned} p &= t_{internal} \\ g &= t_{LE} \\ d &= t_{pd} \end{aligned}$$






# Parasitic Delay ( $t_{internal}$ )

---


- Delay when the output load is zero. Can be obtained by simulation.
- Approximate formula says that the parasitic delay is proportional to  $N$ , the number of inputs in NAND/NOR gates.
- In practice, this is not true if we use a more accurate Elmore delay model. In this case, the parasitic delay grows with  $N^2$ .
- It is not advisable to use more than 4-5 NMOS/PMOS series transistors.
- NMOS in series is always preferred to PMOS in series.
 
# Logical Effort ( $g$ or $t_{LE}$ )


- The ratio of the input capacitance between the current gate and the inverter that can deliver the same output current level.
- Examples (all with unit resistance)



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

 

$$C_{in} = 7$$
$$g = 7/3$$



# Input Waveform Slope

- The largest source of error in the linear model is the slope of the input waveform.
- The delay time formulas can be modified


$$t_{pd} = t_{pd-step} + t_{edge} * k$$

where  $t_{pd-step}$  is the propagation delay assuming step input and  $t_{edge}$  is the input rise/fall time.

- Other sources of error in linear delay model include different input arrival times and parasitic capacitance  $C_{gs}$  and  $C_{gd}$ , and **wire capacitance**.
 
# Stage Ratio

- Very often, large drivers are needed to transmit signals over a long bus or a large load (e.g., output pads and bus driver). This is often achieved by a chain of successively large inverters.
- Usually, we set this ratio to 4.






# 補充教材

---


 
# Optimal Stage Ratio

- The optimal stage ratio (in the sense of least delay) satisfies the equation:  $p_{inv} + \rho(1 - \ln \rho) = 0$ , where  $p_{inv}$  is the parasitic delay and  $\rho$  is the stage ratio.
- The optimal is around 3.59 if  $p_{inv} = 1$ . For convenience 4 is often used. Actually any  $\rho$  between 2.4 and 6 gives a delay that is within 15% of the optimal value.



# Multistage Path Delay

- Example: Chain of gates. Note  $h = C_{out}/C_{in}$ .

$$\begin{aligned}t_{pd-path} &= p_i + g_i * h_i \\&= [1 + (x/10)] + [2 + (5y/3x)] + [2 + 4z/3y)] \\&\quad + [1 + 20/z]\end{aligned}$$

- $p(t_{internal})$  of inverter is 1, and  $p$  of 2-input NAND/NOR is 2. See Table 3.3 of textbook.

