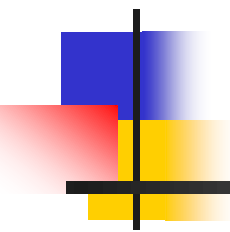


Chapter 7


Sequencing (Sequential Circuit Design)







關志達
台灣大學電機系

Sequencing Elements

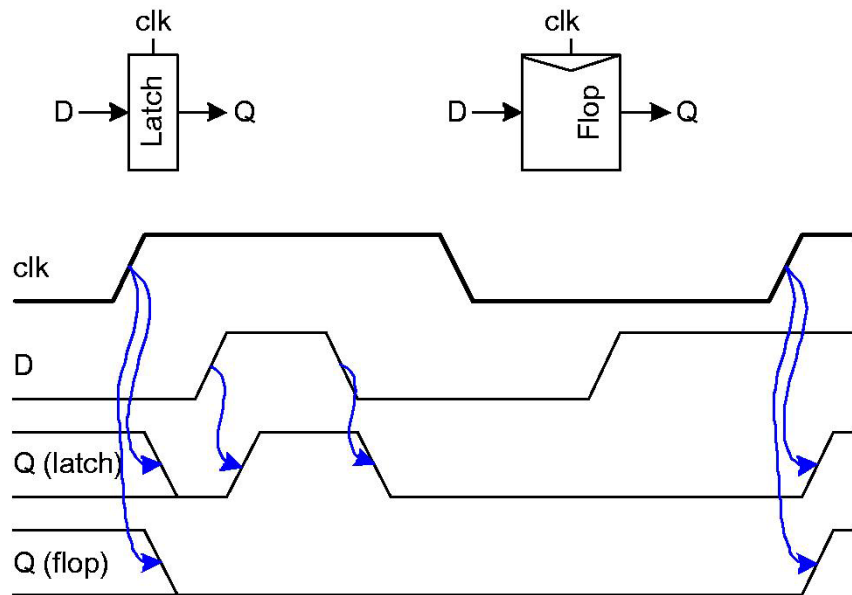- **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
 - a.k.a. master-slave flip-flop, D flip-flop, D register
- Timing diagrams
 - Transparent/opaque




Latch/FF Circuits

 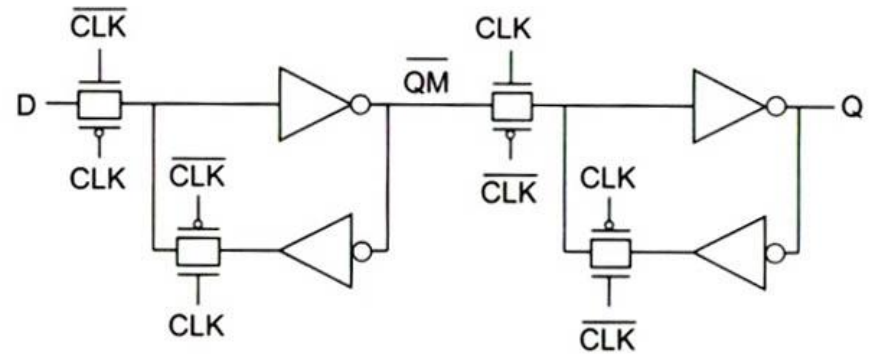  

Latch --- Pass Transistor vs Transmission Gate


■ Pass transistor

 - Simple, low clock loading
- V_t drop
- Non-restoring
- Dynamic
- Bilateral (back-driving),
- Diffusion input (input at S/D),
- Output noise (exposed output)




■ Transmission gate

 - No V_t drop
- Require complementary control inputs
- Larger layout
- Dynamic
- Bilateral (back-driving), diffusion input, exposed output




Latch --- Inverting Buffer

 - Inverting buffer
 - Restoring
 - No backdriving
 - Fixes either output noise sensitivity or diffusion input
 - Inverted output
 - Still dynamic!





Static Latch

 - Static
- Tri-state inverter feedback connection (Fig. 9.18)
- Back-driving risk
- Diffusion input




More Static Latches

  - Buffer-input static
 - No diffusion input
 - Non-inverting
 - Back-driving
- Buffered-input/output static latch
 - No backdriving
 - Widely used in standard cells
 - Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading




Datapath Latch

 - Input noise can be controlled
- Buffered output, unbuffered input.
- Smaller, faster.



Flip-Flop Design

 
- Flip-flop is built as pair of back-to-back latches with complementary clocking signals.
- Dynamic FF
 - Much smaller and simpler
 - Still have clock skew problem that can cause race/hazard.
 - Mainly used in shift register.
 - The clock should go in opposite direction with the signal.



Static FF


■ Static FF


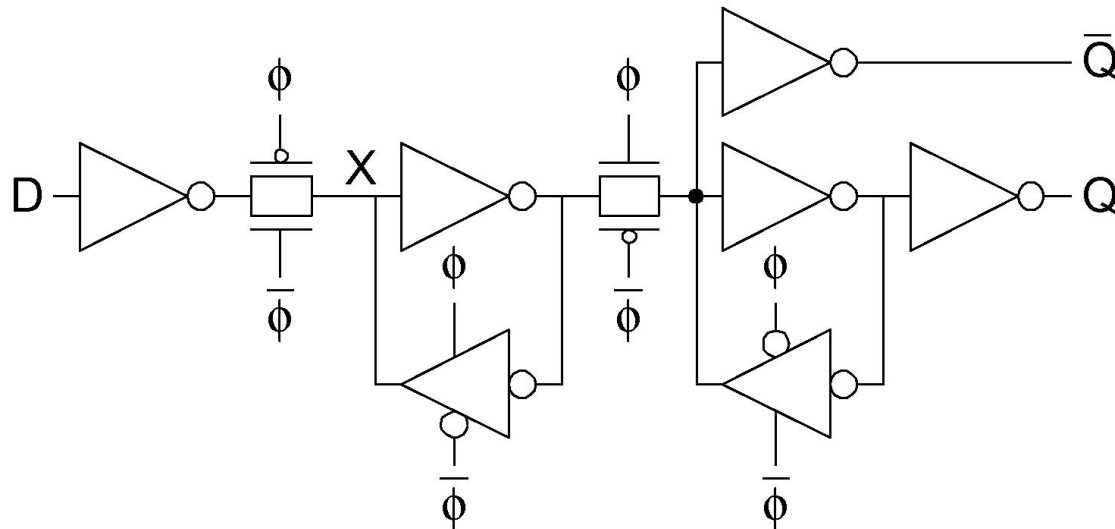
- Used in standard cell library
- Very robust
- Usually the complementary clock is generated locally by an inverter. Without sharp edge, there may be charge sharing.
- May used extra buffer for clock signals to sharpen edges.



Two-Phase Clocking

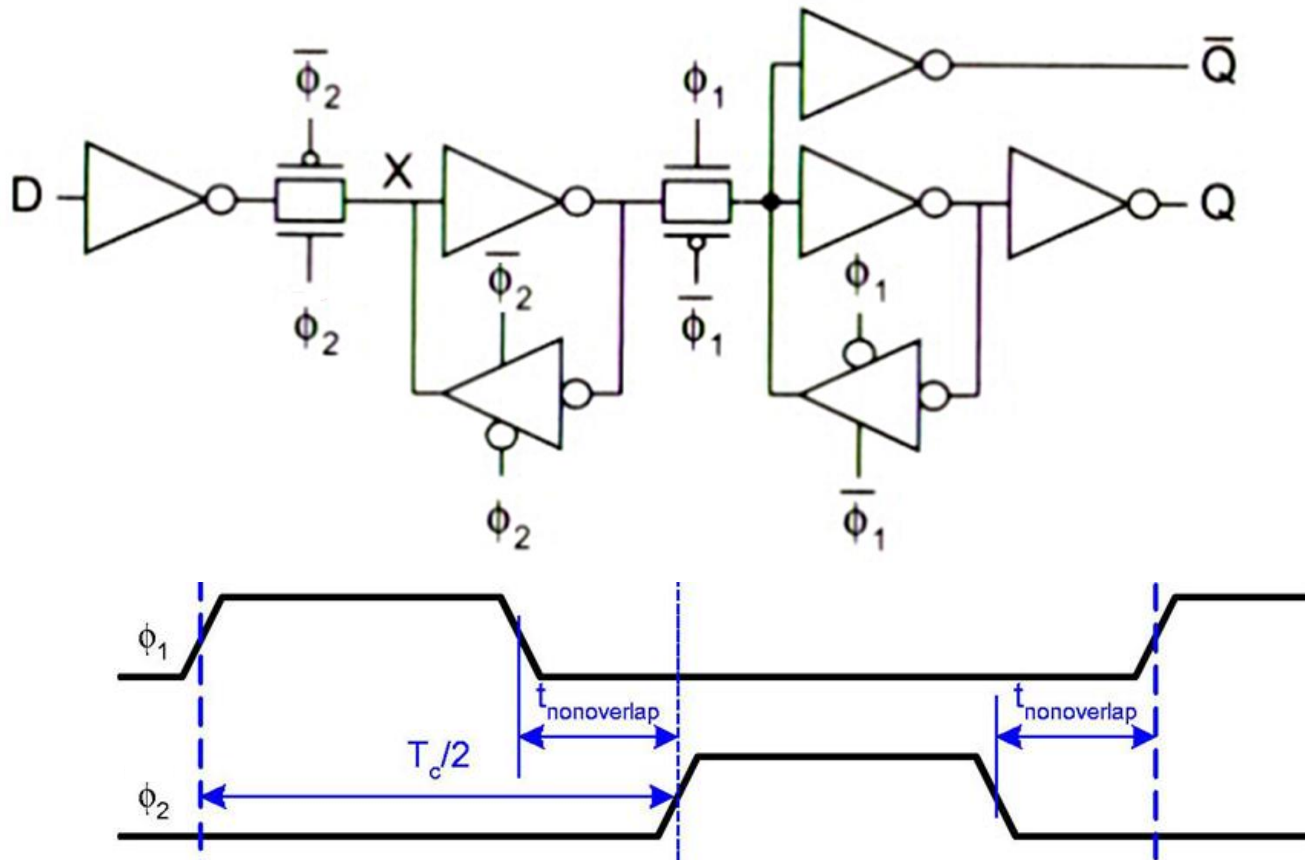- Avoid clock skew problem
- More routing/power for clock signal distribution.




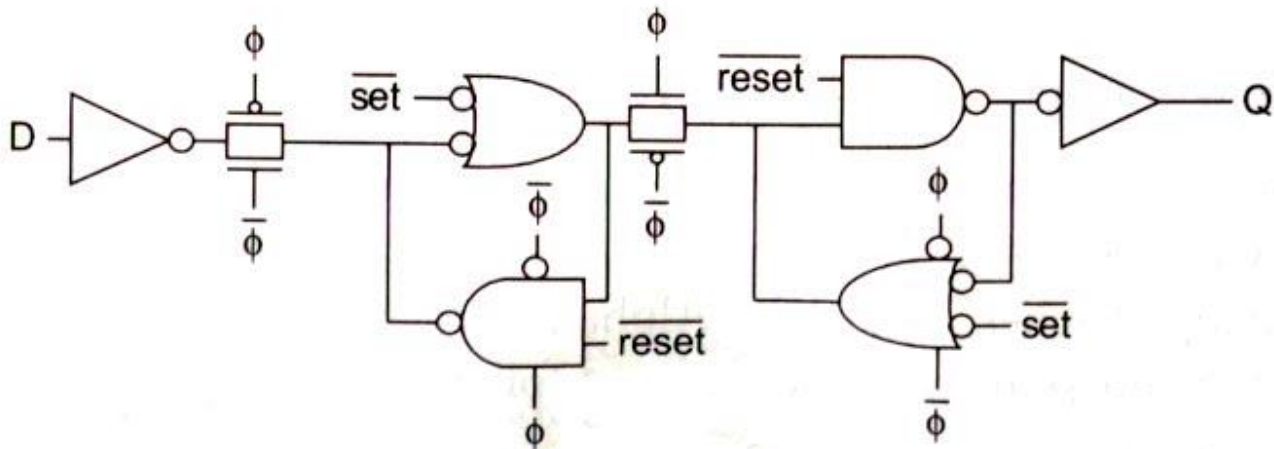 


Enable in FF

- Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: must make sure gated clock is CLEAN, 'en' must be stable when $clk=1$.





Symbol

 

Multiplexer Design

 


Clock Gating Design

    


Sequencing Methods

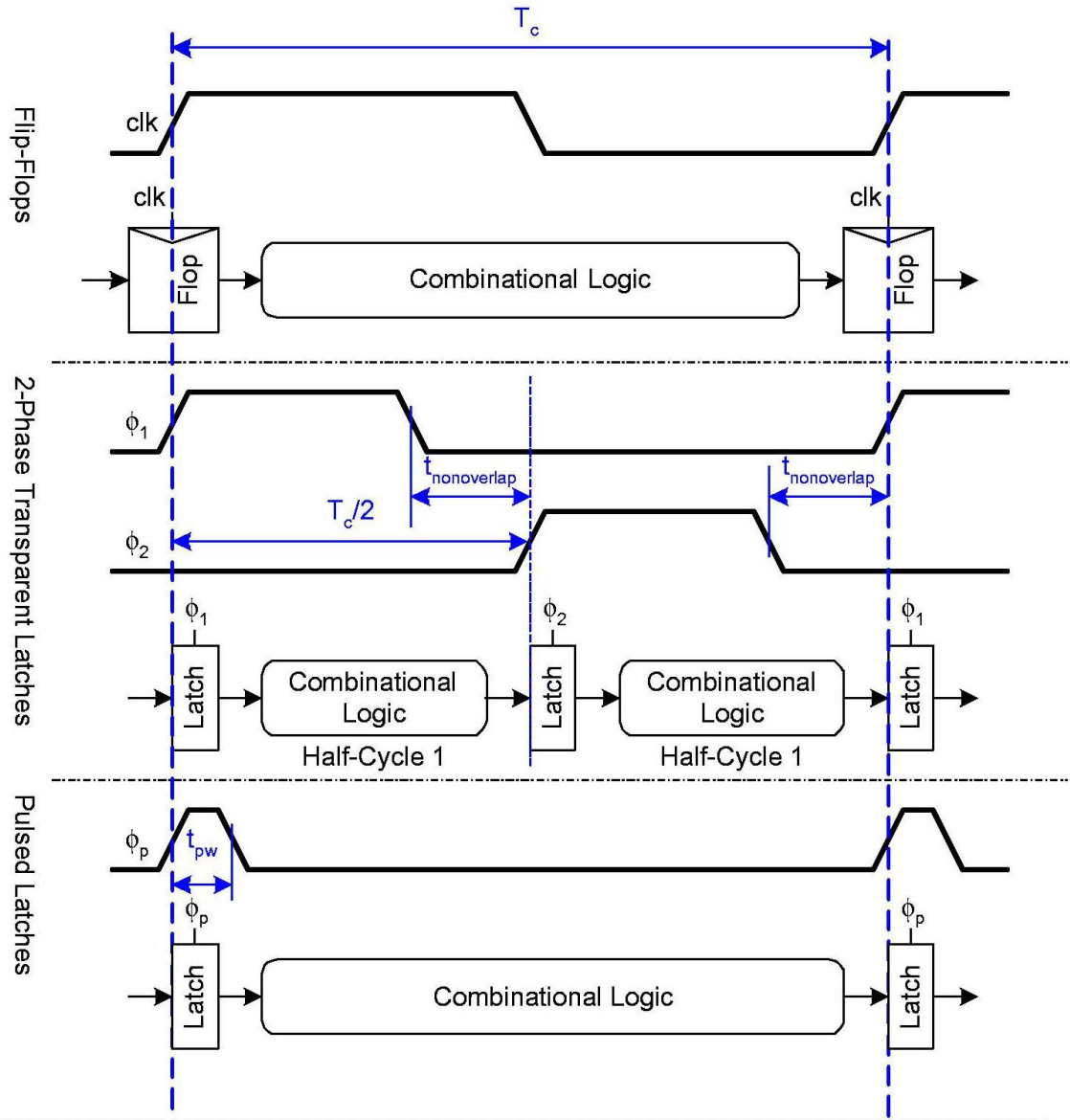- Flip-flops
 - 2-Phase Latches
 - Pulsed Latches
- Similar to gates along a long corridor or canal.









FF-based Sequencing

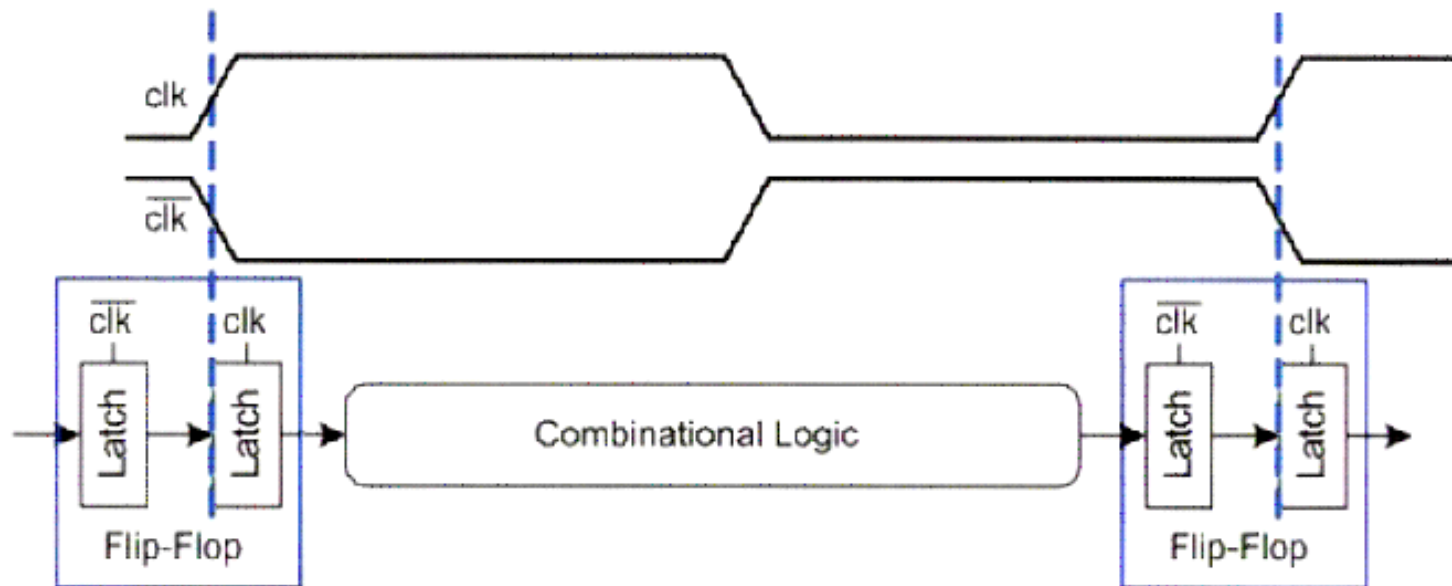- Note that an FF is a pair of back-to-back latches (master-slave).
- At any given time in the FF-based and latch-based methods, one latch is transparent and one latch is opaque.




Timing Diagrams

      

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time


Max-Delay Constraints: FF

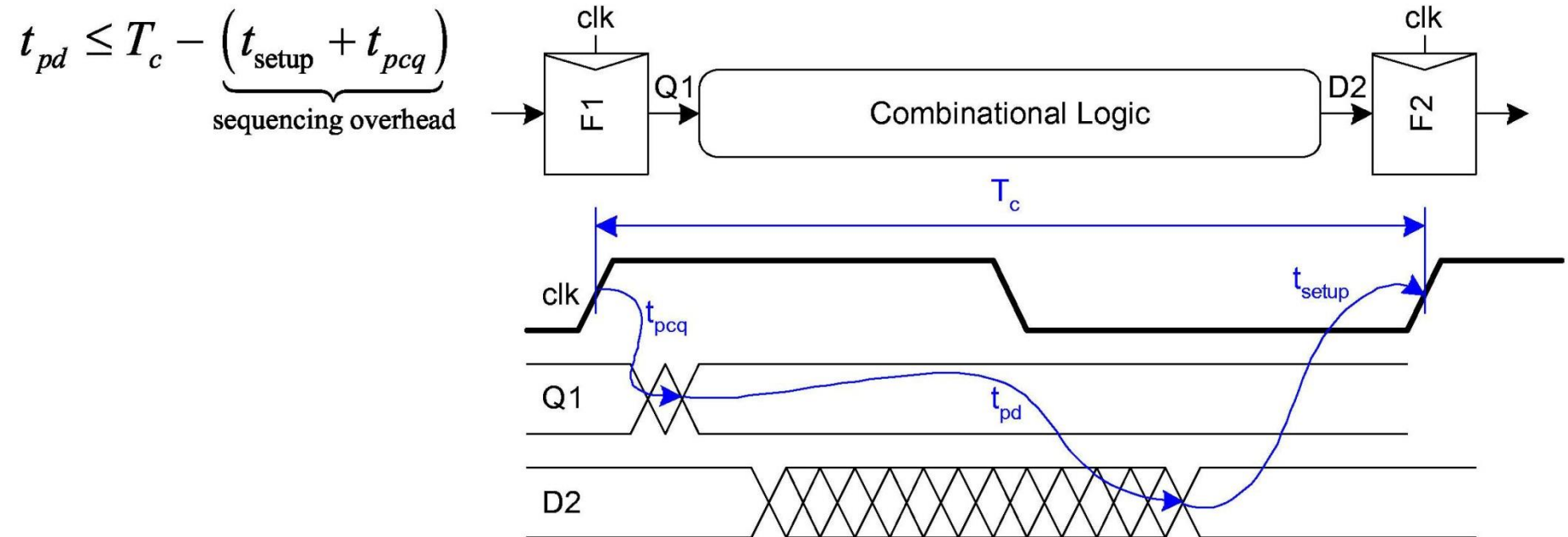- Sequencing overhead decreases the available propagation delay for the combinational logic.



Max-Delay: 2-Phase Latch


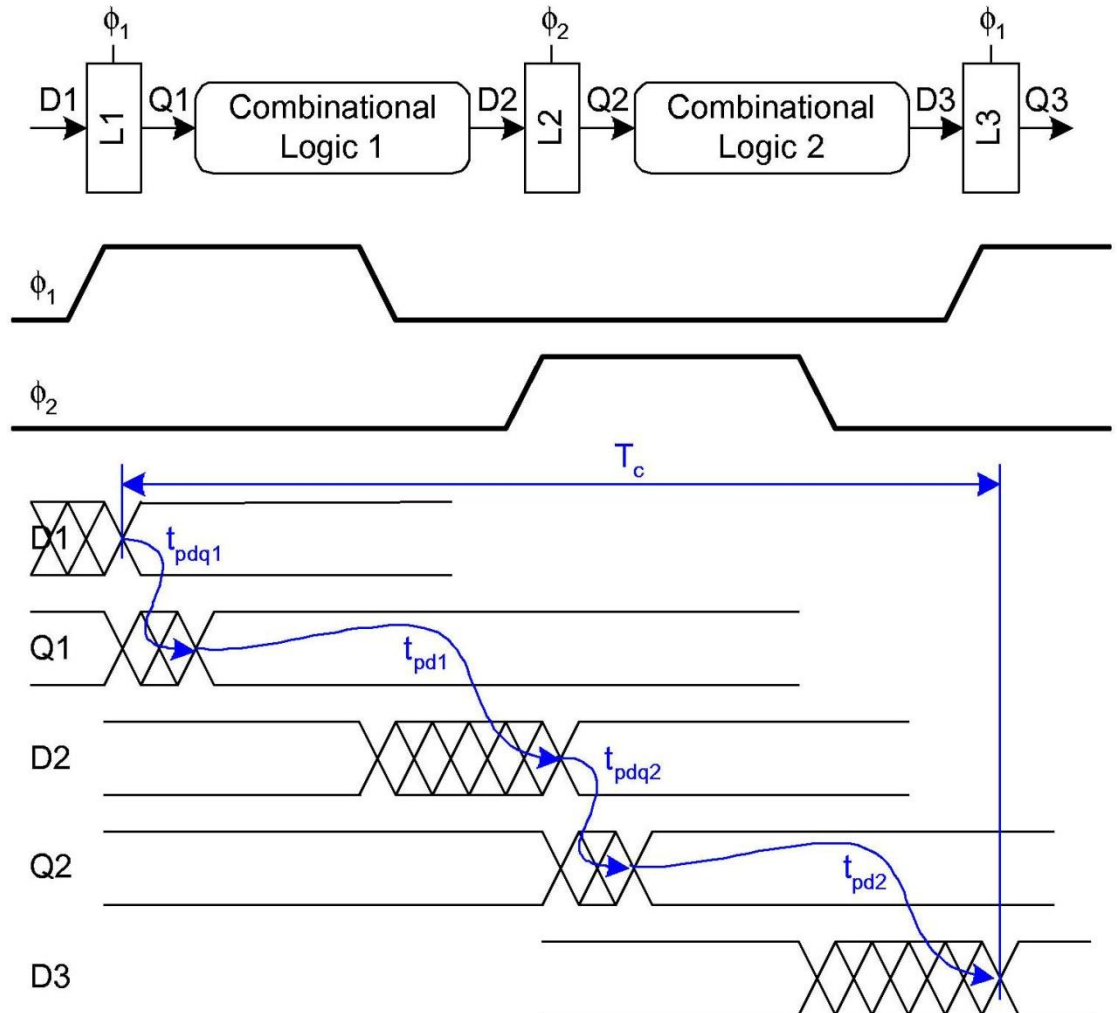
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flop


- If the combinational logic is too fast, the signal can pass two FFs in one cycle.
- Race condition, hold-time failure.
- Worsen with clock skew, e.g. shift registers and scan chain.
  
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$



Min-Delay: 2-Phase Latch
 
$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$






Time Borrowing


- In a flip-flop-based system:
 - A piece of new data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
- FFs have hard edges, i.e. each stage of logic has identical timing limits as others.
- In a latch-based system
 - Data can pass through latch while transparent
 - A stage of logic with longer delay can borrow time from the next stage with shorter delay
 - Must be careful to prevent the total borrowed time from longer than one stage

Time Borrowing Examples

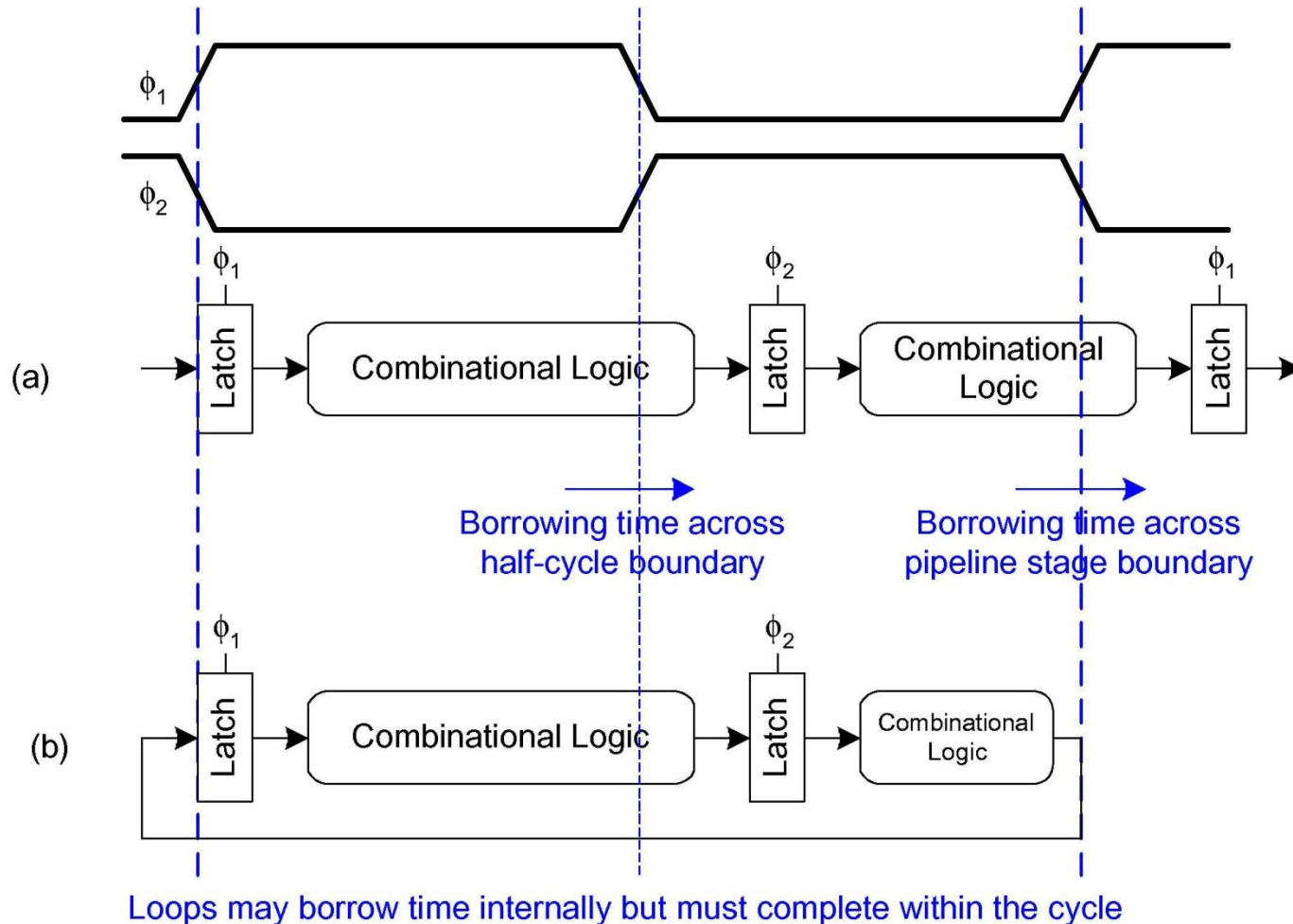


Maximum Time Borrowing
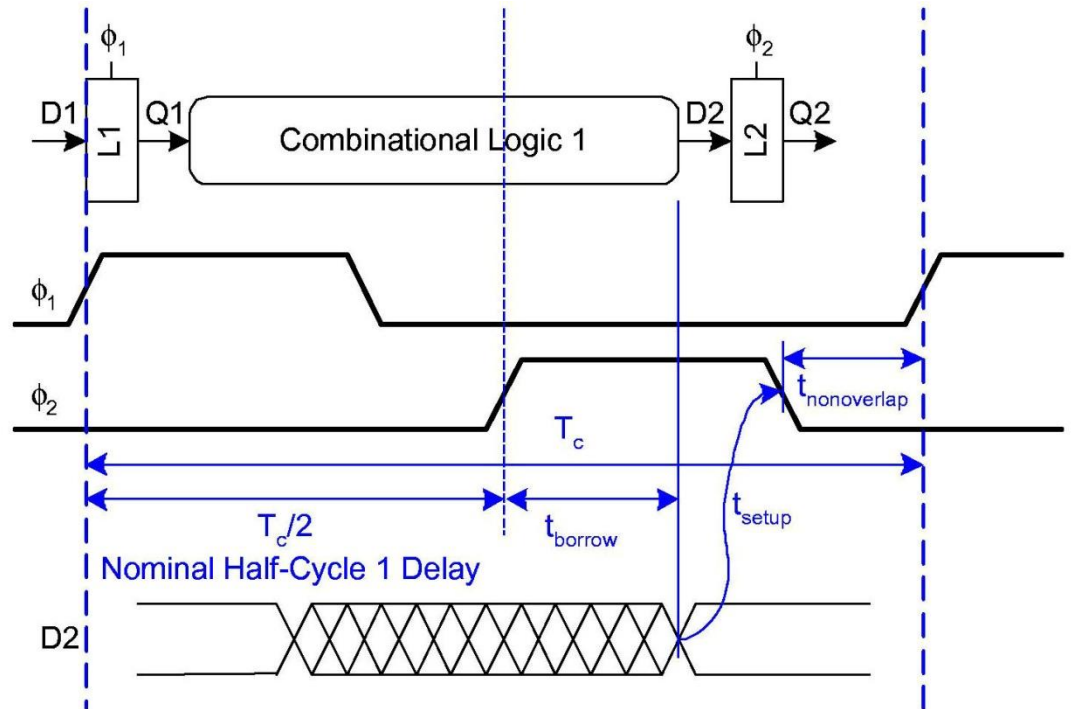
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$



Clock Skew

 - We have assumed zero clock skew
- Clocks actually have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing





Skew: Flip-Flop

- Both delays are worsened by a clock skew time.

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
 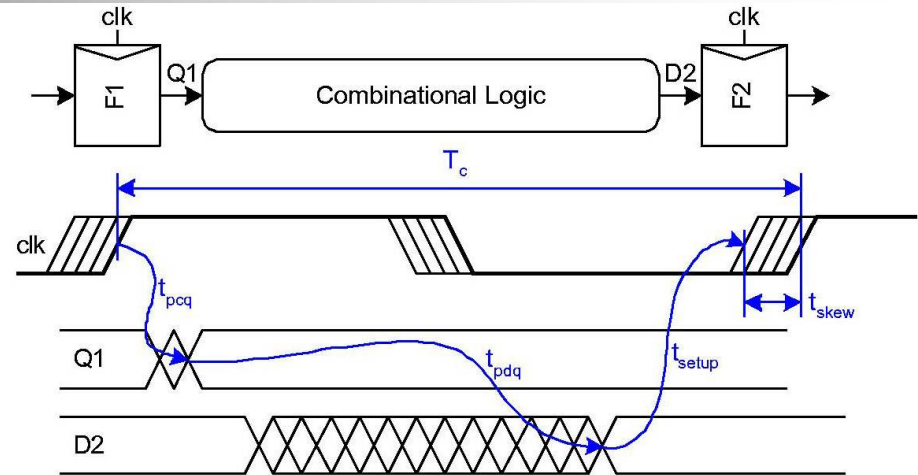
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: 2-Phase Latch

- Propagation delay unchanged.
- Skew tolerant.
- Other two times are worsened by a clock skew time.

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
 
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$





Two-Phase Clocking

- If setup times are violated, increase clock period.
- If hold times are violated, chip fails at any speed.
- A conservative solution to guarantee hold times is to use 2-phase latches with big nonoverlap times.
- With large $t_{\text{nonoverlap}}$, the inequality will always be true.

For latch-based sequencing: $t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$



Adaptive Sequencing

- Designers include timing margin

- Voltage
- Temperature
- Process variation
- Data dependency
- Tool inaccuracies

- Alternative: run faster and check for near failures

  - Idea introduced as "Razor"
 - Basic idea is to sample "D" twice and if the outcomes are different, then "ERR"
 - Increase frequency until at the verge of error
 - Can reduce cycle time by ~30%





Summary

- Flip-Flops:
 - Very easy to use, supported by all tools
- 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing